 


CPU Design Tradeoffs



Maximum Performance: measured by the numbers of instructions executed per second



Minimum Cost : measured by the size of the circuit.



Best Performance/Price: measured by the ratio of MIPS to size. In power-sensitive applications MIPS/Watt is important too.


Processor Performance

- “Iron Law” of performance:


$$\frac{\text{Time}}{\text{Program}} = \frac{\text{Instructions}}{\text{Program}} \cdot \frac{\text{Cycles}}{\text{Instruction}} \cdot \frac{\text{Time}}{\text{Cycle}} \qquad \text{Perf} = \frac{1}{\text{Time}}$$

- Options to reduce execution time:
 - Executed instructions ↓ (work/instruction ↑)
 - Cycles per instruction (CPI) ↓
 - Cycle time ↓ (frequency ↑)
- Today: Simple, CPI=1 but low-frequency Beta
 - Later: Pipelining to increase frequency

Reminder: Beta ISA

 

 Operate class: $\text{Reg}[Rc] \leftarrow \text{Reg}[Ra] \text{ op } \text{Reg}[Rb]$



Operate class: $\text{Reg}[Rc] \leftarrow \text{Reg}[Ra] \text{ op } \text{SXT}(C)$

Opcodes, both formats:

ADD	SUB	MUL*	DIV*	*optional
CMPEQ	CMPLT			
AND	OR	XOR	XNOR	
SHL	SHR	SRA		



LD: $\text{Reg}[Rc] \leftarrow \text{Mem}[\text{Reg}[Ra] + \text{SXT}(C)]$

ST: $\text{Mem}[\text{Reg}[Ra] + \text{SXT}(C)] \leftarrow \text{Reg}[Rc]$

LDR: $\text{Reg}[Rc] \leftarrow \text{Mem}[\text{PC} + 4 + 4 * \text{SXT}(C)]$

BEQ: $\text{Reg}[Rc] \leftarrow \text{PC} + 4$; if $\text{Reg}[Ra] = 0$ then $\text{PC} \leftarrow \text{PC} + 4 + 4 * \text{SXT}(C)$

BNE: $\text{Reg}[Rc] \leftarrow \text{PC} + 4$; if $\text{Reg}[Ra] \neq 0$ then $\text{PC} \leftarrow \text{PC} + 4 + 4 * \text{SXT}(C)$

JMP: $\text{Reg}[Rc] \leftarrow \text{PC} + 4$; $\text{PC} \leftarrow \text{Reg}[Ra]$

Instruction classes distinguished by
OPCODE:

OP

OPC

MEM

Control Flow


Approach: Incremental Featurism

We'll implement datapaths for each instruction class individually, and merge them (using MUXes, etc)


Steps:

1. ALU instructions
2. Load & store instructions
3. Jump & branch instructions
4. Exceptions

Component Repertoire:

 


Multi-Ported Register File

 

Register File Timing

 2 **combinational** READ ports, 1 **clocked** WRITE port




What if (say) $WA=RA1$???

RD1 reads "old" value of $Reg[RA1]$ until next clock edge!

ALU Instructions

32-bit (4-byte) ADD instruction:

 


Means, to Beta, $Reg[R4] \leftarrow Reg[R2] + Reg[R3]$

Need hardware to:

- **FETCH** (read) 32-bit instruction for the current cycle
- **DECODE** instruction: ADD, SUB, XOR, etc
- **READ** operands (Ra, Rb) from Register File
- **EXECUTE** operation
- **WRITE-BACK** result into Register File (Rc)


Instruction Fetch/Decode

 Use a counter to FETCH the next instruction: PROGRAM COUNTER (PC)




- Use PC as memory address
- Add 4 to PC, load new value at end of cycle
- Fetch instruction from memory
- Use some instruction fields directly (register numbers, 16-bit constant)
- Use bits [31:26] to generate control signals


ALU Op Datapath

 



ALU Op Datapath

 

ALU Operations (with constant)

 

  
Operate class: $\text{Reg}[Rc] \leftarrow \text{Reg}[Ra] \text{ op } \text{SXT}(C)$



Sign-extension requires no logic...



 Just replicate ID[15] sixteen times to create high-order bits!



$C: \text{SXT}(\text{ID}[15:0])$

32

1 0 BSEL




BSEL


ALUFN

WERF


ALU Operations (with constant)

 


Load Instruction

 


Load Instruction

 


Store Instruction

 

Store Instruction

 


JMP Instruction

 


JMP Instruction

0 1 1 0 1 1	Rc	Ra	Literal C (signed)
-------------	----	----	--------------------

 
JMP: $\text{Reg}[Rc] \leftarrow PC+4$; $PC \leftarrow \text{Reg}[Ra]$



BEQ/BNE Instructions

 

BEQ/BNE Instructions

 

Load Relative Instruction

0 1 1 1 1 1	Rc	Ra	Literal C (signed)
-------------	----	----	--------------------

LDR: $\text{Reg}[Rc] \leftarrow \text{Mem}[\text{PC} + 4 + 4 * \text{SXT}(C)]$

What's Load Relative good for anyway??? I thought

- Code is “PURE”, i.e. READ-ONLY; and stored in a “PROGRAM” region of memory;
- Data is READ-WRITE, and stored either
 - On the STACK (local); or
 - In some GLOBAL VARIABLE region; or
 - In a global storage HEAP.

So why have an instruction designed to load data that's “near” the instruction???

Addresses & other large constants

C: X = X * 123456;

BETA:

LD(X, r0)

LDR(c1, r1)


MUL(r0, r1, r0)

ST(r0, X)


...

c1: LONG(123456)

LDR Instruction

 

LDR Instruction

 

Exceptions


- What if something bad happens?
 - Execution of an illegal opcode
 - Reference to non-existent memory
 - Divide by zero
- Or maybe just something unanticipated
 - User hits a key
 - A packet comes in via the network
- Exceptions let us handle these cases in software:
 - Treat each case as an (implicit) procedure call
 - Procedure handles problem, returns to interrupted program
 - Transparent to interrupted program!
 - Important added capability: handlers for certain errors (illegal opcodes), can extend ISA using software

Exception Processing

- Plan:
 - Interrupt running program
 - Invoke exception handler (like a procedure call)
 - Return to continue execution
- Exception and interrupt terms often used interchangeably, with minor distinctions:
 - **Exceptions** usually refer to **synchronous events**, generated by program (e.g., illegal instruction, divide-by-0, illegal address)
 - **Interrupts** usually refer to **asynchronous events**, generated by I/O devices (e.g., keystroke, packet received, disk transfer complete)


Exception Implementation

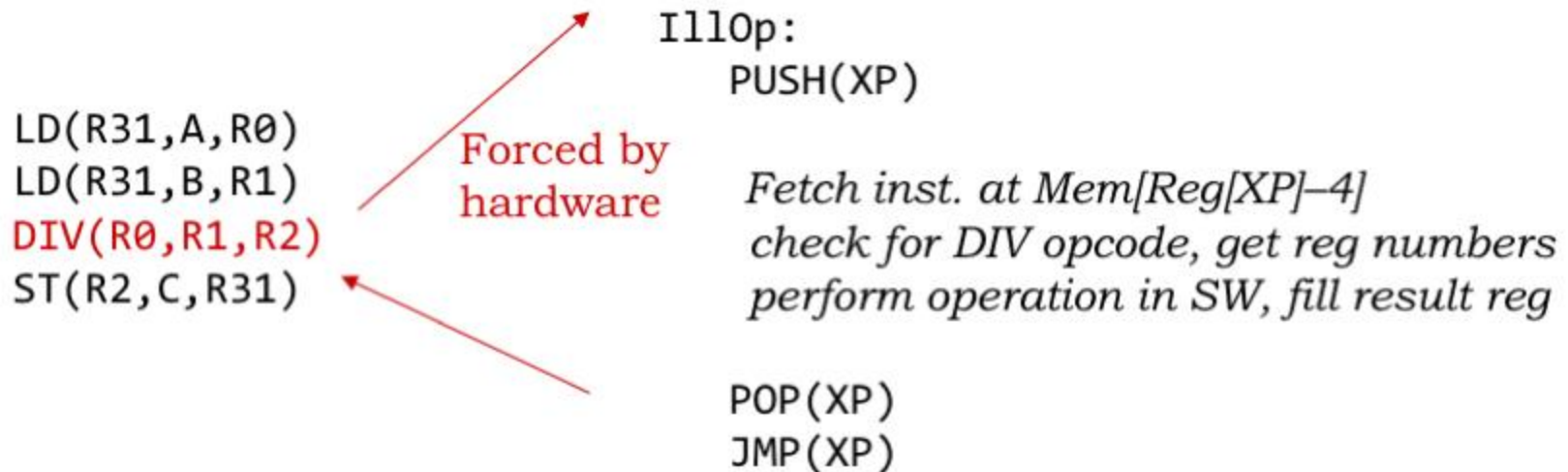- Instead of executing instruction, fake a procedure call
 - Save current PC+4 (as branches do)
 - Load PC with exception vector: 0x4 for synchronous events, 0x8 for asynchronous events
- We save PC+4 in register R30 (which we call XP)
 - ... and prohibit programs from using XP (why?)
- Example: DIV unimplemented




Exceptions

 Bad Opcode: $\text{Reg}[\text{XP}] \leftarrow \text{PC}+4$; $\text{PC} \leftarrow \text{"I11Op"}$
 Other: $\text{Reg}[\text{XP}] \leftarrow \text{PC}+4$; $\text{PC} \leftarrow \text{"Xadr"}$




Exceptions

 Bad Opcode: $\text{Reg}[XP] \leftarrow \text{PC}+4$; $\text{PC} \leftarrow \text{"I11Op"}$
 Other: $\text{Reg}[XP] \leftarrow \text{PC}+4$; $\text{PC} \leftarrow \text{"Xadr"}$



Beta: Our “Final Answer”

 

Control Logic

	RESET	IRQ	OP	OPC	LD	LDR	ST	JMP	BEQ	BNE	ILLOP
ALUFN	--	--	F(op)	F(op)	"+"	"A"	"+"	--	--	--	--
ASEL	--	--	0	0	0	1	0	--	--	--	--
BSEL	--	--	0	1	1	--	1	--	--	--	--
MOE	--	--	--	--	1	1	0	--	--	--	--
MWR	0	0	0	0	0	0	1	0	0	0	0
PCSEL	--	4	0	0	0	0	0	2	Z ? 1 : 0	Z ? 0 : 1	3
RA2SEL	--	--	0	--	--	--	1	--	--	--	--
WASEL	--	1	0	0	0	0	--	0	0	0	1
WDSEL	--	0	1	1	2	2	--	0	0	0	0
WERF	--	1	1	1	1	1	0	1	1	1	1

Implementation choices:

- 64-location ROM indexed by opcode with external logic to handle changes due to Z and IRQ inputs
- Entirely combinational logic (faster, but much more work!)

*Is **that** all
there is to
building a
processor???*



*No.
You've gotta print
up all those little
"Beta Inside"
stickers.*

